



## INDEX

EXP. NO.	DATE	TITLE	PAGE	REMARKS
01	20/02/23	To verify Kirchoff's Voltage Law (KVL) in D.C. circuits.	01-04	KmtBlk 27/02/23 X
02	27/02/23	To verify Kirchoff's current law (KCL) in D.C. circuits	05-08	KmtBlk 13/03/23 B+
03	13/03/23	To verify superposition theorem for D.C. circuits	09-12	KmtBlk 20/03/23 X
04	20/03/23	To verify Thevenin's Theorem for D.C. circuits.	13-16	KmtBlk 27/03/23 X+
05	03/04/23	To verify Norton's Theorem for D.C. circuits.	17-20	

## Experiment No. - 01

Objective :

To verify Kirchhoff's voltage law (KVL) in D.C. circuits.

Theory :

Kirchhoff's Voltage Law (KVL) : This law states that at any instant (time). The algebraic sum of the voltages taken in the same direction around a loop (closed path) is zero. In other words, the net voltage around a closed circuit is zero. Mathematically it can be expressed as:


$$\sum V_k = 0$$

This law is valid regardless of the direction in which loop is considered. It should also be noted that in a circuit, the direction of a loop does not have to be the same as the direction of current. However, the sign convention is very important.

Guru

Teacher's Signature

Circuit Diagram:

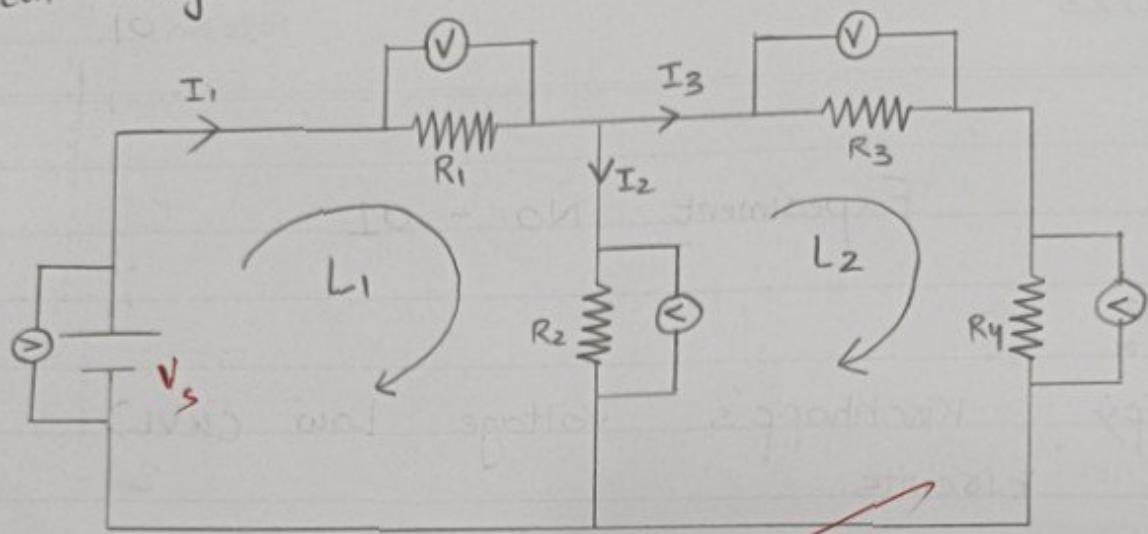

$$R_1 \rightarrow (510 \pm 1\%) \Omega$$

$$R_2 \rightarrow (47 \pm 5\%) \Omega$$

$$R_3 \rightarrow (750 \pm 1\%) \Omega$$

$$R_4 \rightarrow (470 \pm 5\%) \Omega$$

## Apparatus Required :

S.No	Name	Range	Quantity
1.	DC Voltmeter	0-20 V	1
2.	Breadboard	-	1
3.	Connecting Wires	-	4
4.	Carbon Resistors	(47 - 750) $\Omega$	4

## Equations :

According to KVL, for the given circuit in Loop 1:

$$V_s - I_1 R_1 - I_2 R_2 = 0$$

OR

$$V_s = I_1 R_1 + I_2 R_2$$

OR

$$V_s = V_1 + V_2$$

Similarly, for Loop 2 :

$$I_2 R_2 = I_3 R_3 + I_3 R_4 \quad \text{OR}$$

$$V_2 = V_3 + V_4$$

GuruD

Teacher's Signature

Procedure :

- 1.) Connect the circuit as shown in circuit diagram.
- 2.) Switch on the power supply.
- 3.) Note the Reading of Voltmeter.

Observation Table :

S. No.	$V_s$ (V)	$V_1$ (V)	$V_2$ (V)	$V_3$ (V)	$V_4$ (V)	$V_s = V_1 + V_2$	$V_2 = V_3 + V_4$
1.	2.00	1.81	0.15	0.09	0.06	1.96	0.15
2.	5.00	4.52	0.40	0.24	0.15	4.92	0.39
3.	10.01	9.07	0.79	0.49	0.30	9.86	0.79
4.	12.01	10.91	0.95	0.59	0.36	11.86	0.95

Result :

The KVL is verified.

Teacher's Signature \_\_\_\_\_

### Precaution :

- 1.) All connections should be tight.
- 2.) Before connecting the instruments check their zero reading.
- 3.) The terminals of the ~~resistance~~ should be properly connected.

### Learning Outcomes :

- 1.) We learnt to create circuit on breadboard.
- 2.) We learnt colour coding of different resistors.
- 3.) We learnt about KVL and verified it.

### Applications :

- 1.) KVL is used to calculate the unknown values of current and voltages in the circuit.
- 2.) The Wheatstone bridge is an essential application of Kirchoff's Law. It is also used in mesh and node analysis.
- 3.) KVL helped in analysis and calculation of complex circuits.

Given

Teacher's Signature

(X) R-L-Bhatt  
27/10/23

## Experiment No. - 02

Objective :

To verify Kirchhoff's current Law (KCL) in D.C. circuits.


Theory :

Kirchhoff's current Law (KCL) :

This law states that the algebraic sum of the currents into a node or a junction at any instant is zero. In other words, the sum of currents entering the node is equal to the sum of currents leaving the node. Mathematically, it can be expressed as

$$\sum I_K = 0$$

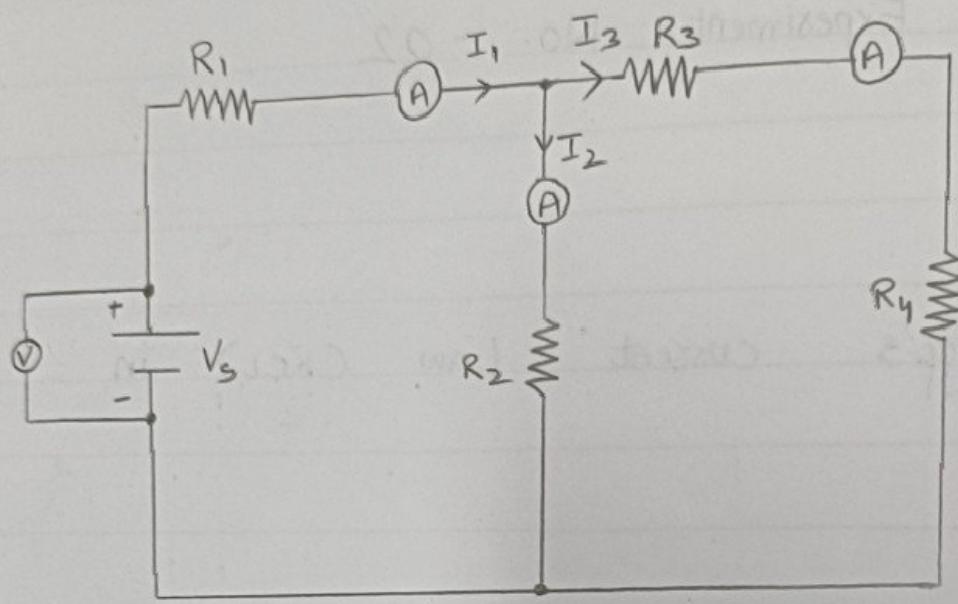If the current leaving the node is taken as positive (+ve), then the current entering the node should be taken as negative (-ve) or vice-versa.



Circuit Diagram for Verification of KCL

$$R_1 \rightarrow (560 \pm 5\%) \Omega$$

$$R_2 \rightarrow (47 \pm 5\%) \Omega$$

$$R_3 \rightarrow (680 \pm 5\%) \Omega$$

$$R_4 \rightarrow (220 \pm 5\%) \Omega$$

## Apparatus Required :

S.No	Name	Range	Quantity
01.	DC Voltmeter	(0-20) V	1
02.	DC Ammeter	(0-50) mA	1
03.	Breadboard	-	1
04.	Connecting Wires	-	6
05.	Carbon Resistors	(47-680) $\Omega$	4

## Equations :

According to KCL, for the given circuit at node 'a' :

$$I_1 = I_2 + I_3$$

## Procedure :

- 1.> Connect the circuit as shown in circuit diagram.
- 2.> Switch on the power supply.
- 3.> Note the Reading of ammeter.

## Observation Table :

S.No	$V_s$ (V)	$I_1$ (mA)	$I_2$ (mA)	$I_3$ (mA)	$I_1 = I_2 + I_3$
01.	2	3.3	3.1	0.1	3.2 ✓
02.	5	8.3	7.9	0.3	8.2 ✓
03.	8	13.4	12.7	0.6	13.3 ✓
04.	12	20.2	19.2	0.9	20.1 ✓

## Result :

The KCL is verified. ✓

## Precaution :

- 1.) All connections should be tight.
- 2.) Before connecting the instruments check their zero reading.
- 3.) The terminals of the resistance should be properly connected.

## Learning Outcomes :

- 1.) We learnt to create circuit on breadboard.

- 2.) We learnt colour coding of different resistors.
- 3.) We learnt about KCL and verified it by implementing a circuit.

### Applications :

- 1.) KCL is used to calculate the unknown values of current and voltages in the circuit.
- 2.) The wheatstone bridge is an essential application of Kirchoff's Law. It is also used in mesh and node analysis.
- 3.) KCL helped in analysis and calculation of complex circuits.

BT

Welt Blatt  
13/03/23

Experiment No. - 03

Aim :

To verify superposition theorem for D.C. circuits.

Theory :

In a linear bilateral network containing more than one source, the current flowing through any branch is the algebraic sum of the currents flowing through that branch by considering one source at a time and replacing the other sources by their internal resistance.

Apparatus Required :

S. No.	Name	Range	Quantity
01>	D.C Voltmeter	0-20 V	1
02>	D.C Ammeter	0-200 mA	1
03>	Breadboard	-	1
04>	Connecting Wires	-	6
05>	Carbon Resistors	(270 - 560) $\Omega$	3

Guru

Teacher's Signature

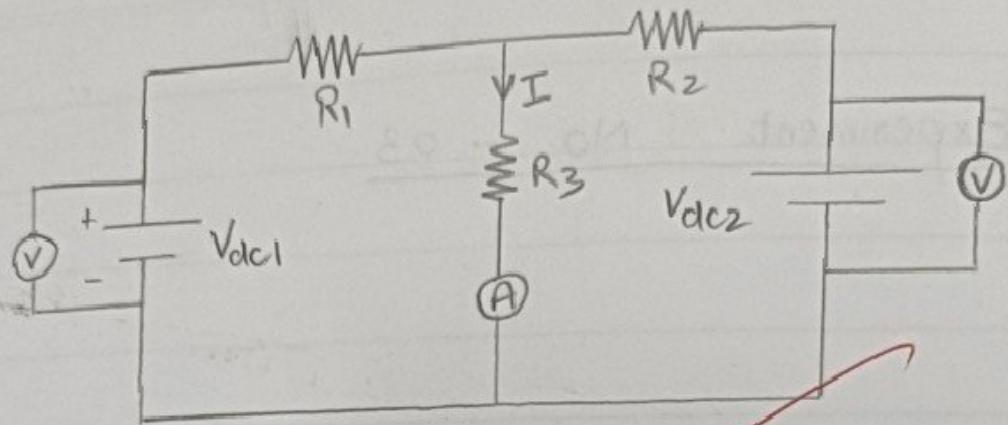


Fig. - 3.1


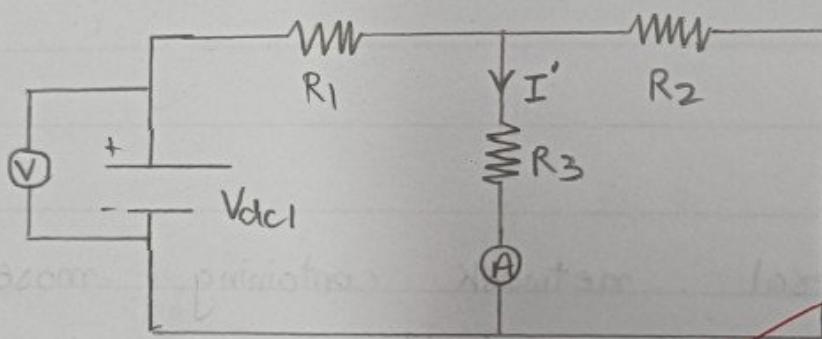


Fig. - 3.2

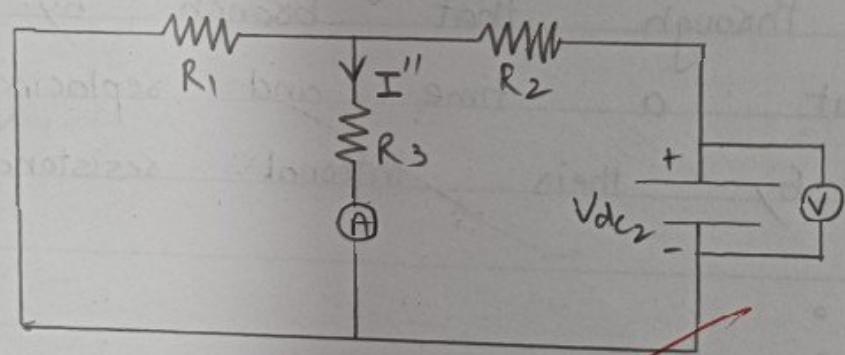

$$R_1 \rightarrow 560 \pm 5\% \Omega$$

$$R_2 \rightarrow 330 \pm 5\% \Omega$$

$$R_3 \rightarrow 270 \pm 5\% \Omega$$

### Procedure :

- 1.) Connect the circuit diagram as per the circuit diagram shown in Fig. 3.1.
- 2.) Switch on the DC power supplies ( $V_1$ ) and ( $V_2$ ) say 5V and 10V and note down the corresponding ammeter reading  $I$ .
- 3.) Replace the second power supply  $V_2$  by short circuit (Fig. 3.2).
- 4.) Switch on the power supply  $V_1$  and note down the corresponding ammeter reading ' $I$ '.
- 5.) Connect the second power supply  $V_2$  and replace  $V_1$  power supply by short circuit (Fig. 3.3).
- 6.) Switch on the power supply  $V_2$  and note down the corresponding reading  $I''$ .
- 7.) Verify the following condition

$$I = I' + I''$$

## Observation Table :

S. No.	V <sub>d1</sub> (V)	V <sub>d2</sub> (V)	Measured Value I (mA)	I' (mA)	I'' (mA)	Calculated Value $I = I' + I''$ (mA)
01	2.01	3.01	5.6	1.6	4.0	5.6
02	5.02	7.02	13.3	4.0	9.3	13.3
03	7.00	9.02	17.6	5.5	12.0	17.5
04	9.02	11.00	21.9	7.2	14.7	21.9

## Conclusion :

Hence, Superposition theorem for given circuit is verified.

## Precaution :

1. All connections should be tight and perfect.
2. Connect the DC meters with proper polarity.
3. Readings must be well within the range of the meters.

## Learning Outcomes :

1. We learnt to create circuit on breadboard.

Guru

Teacher's Signature \_\_\_\_\_

- 2.) We learnt colour coding of different resistors.  
3.) We learnt about superposition theorem and verified it experimentally.

### Applications :

The application of superposition theorem is, we can employ only linear circuits as well as the circuit which has more supplies.

(X)

Mohit Bhatt  
20/03/23

## Experiment No. - 04

Aim :

To verify Thevenin's theorem for DC circuits.

Theory :

It states that, any two-terminal, linear, bilateral network can be replaced by an equivalent circuit consisting of a voltage source in series with the resistance (impedance) seen from that terminals. The equivalent voltage source,  $V_{Th}$  is the open circuit voltage between the terminals and equivalent Resistance,  $R_{Th}$  is also the resistance measured by looking back into the network from the open circuit terminals by replacing all the sources by their internal resistances.

Formula :

$$\text{Load current } (I_L) = \frac{V_{Th}}{R_{Th} + R_L}$$

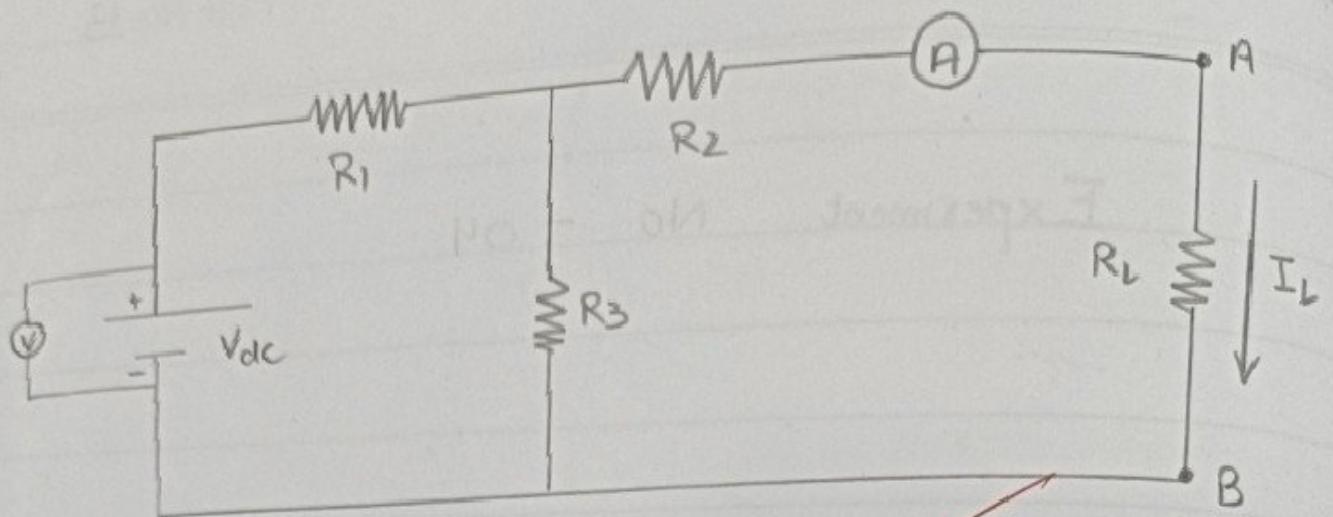


Fig. 4.1 Connection Diagram of Thevenin's Theorem

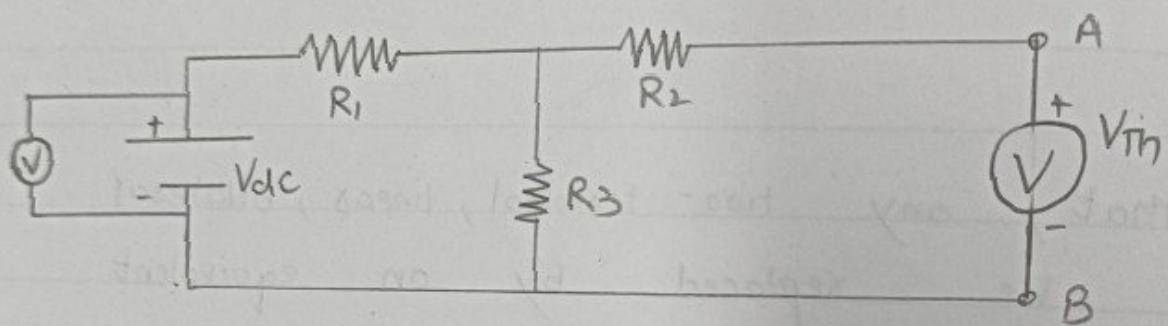


Fig. 4.2 Measurement of  $V_{Th}$

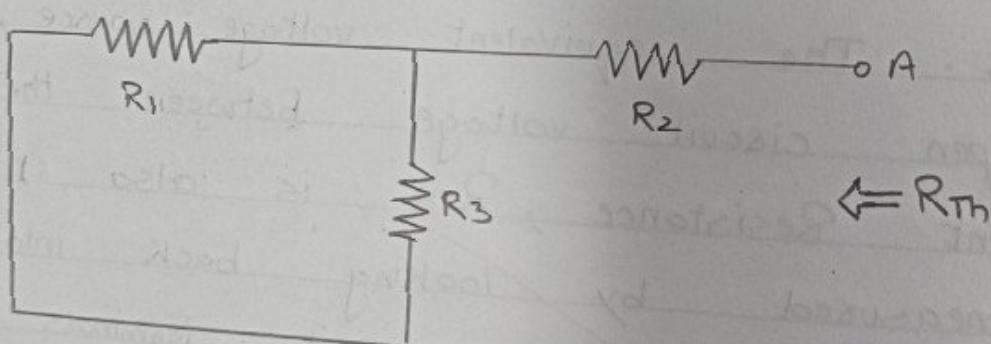


Fig. 4.3 Measurement of  $R_{Th}$

$$R_1 \rightarrow (330 \pm 1\%) \Omega$$

$$R_2 \rightarrow (750 \pm 1\%) \Omega$$

$$R_3 \rightarrow (330 \pm 1\%) \Omega$$

$$R_L \rightarrow (750 \pm 1\%) \Omega$$

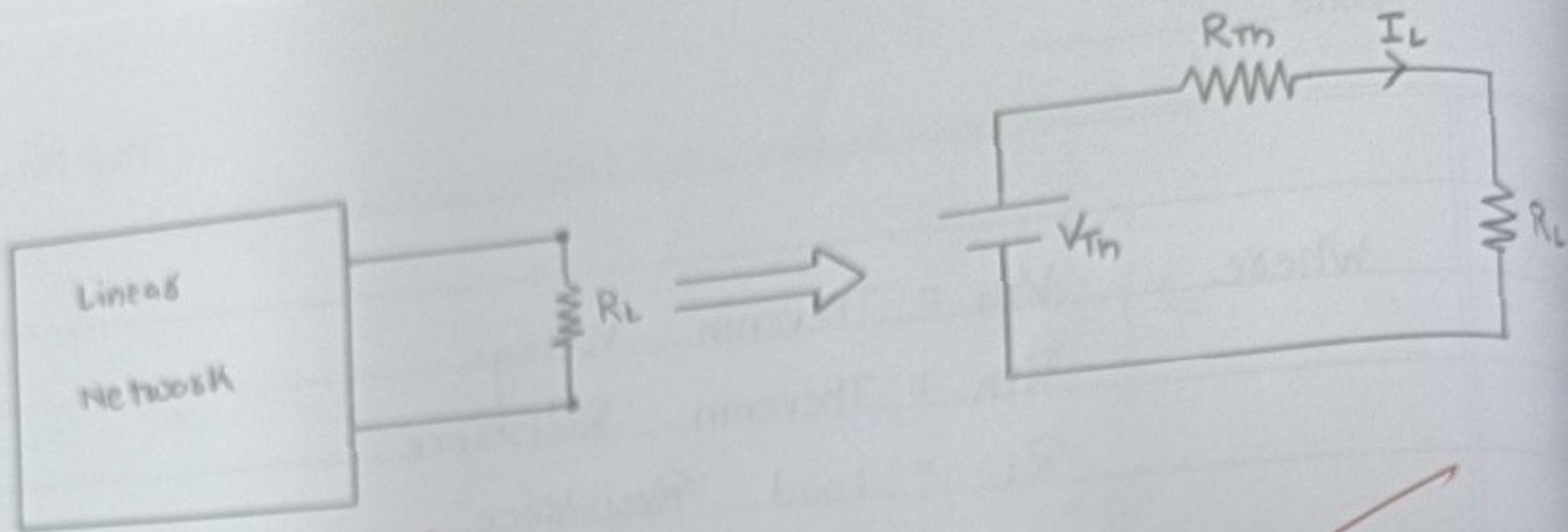


Fig. 4.4 Thevenin's Equivalent Circuit

Where

 $V_{Th}$  = Thevenin Voltage $R_{Th}$  = Thevenin Resistance $R_L$  = Load Resistance

Apparatus Required :

S. No.	Name	Range / Value	Quantity
01. >	DC Voltmeter	0 - 20 V	1
02. >	DC Ammeter	0 - 200 mA	1
03. >	Breadboard	—	1
04. >	Connecting Wires	—	8
05. >	Carbon Resistors	(330 - 750) $\Omega$	4

Procedure :

01. > The circuit is connected as shown in Fig. 4.1.
02. > Note the reading of ammeter which is load current in the circuit.
03. > Find the Open circuit voltage across the terminal AB when load Resistance is removed (Fig. 4.2).
04. > Measure the Thevenin's resistance by using Fig. 4.3.
05. > Compute the current flowing through  $R_L$  (Fig. 4.4) using the equation.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

And Compare the first reading

Observation Table :

S. No.	V <sub>dc</sub> (Volts)	I <sub>L</sub> (mA)	R <sub>L</sub> (Ω)	V <sub>Th</sub> (Volts)	R <sub>Th</sub> (Ω)	I <sub>L</sub> = V <sub>Th</sub> / (R <sub>Th</sub> + R <sub>L</sub> ) (mA)
01>	3	0.7	752	0.93	562	0.7
02>	5	1.1	752	1.55	562	1.17
03>	7	1.6	752	2.17	562	1.65
04>	10	2.3	752	3.09	562	2.35

Conclusion :

Hence, Thevenin's theorem is verified for D.C. circuits.

### Precaution :

- 01.) As the input is ON on DC supply, use only the DC meters.
- 02.) Connect the DC meters with proper polarity.
- 03.) Connect the circuit as per the diagram.
- 04.) All connections must be tight and proper.

### Learning Outcomes :

- 01.) We learnt to create circuit on Breadboard.
- 02.) We learnt colour coding of different resistors.
- 03.) We learnt about Thevenin's Theorem and verified it.

### Applications :

- 01.) Thevenin's theorem is used in the analysis of power systems.
- 02.) Thevenin's theorem is used in source modelling and resistance measurement using the wheatstone bridge.

(+)   
 27/03/23

Wheatstone  
27/03/23

## Experiment No. - 05

Aim :

To verify Norton's theorem for DC circuits.

Theory :

It states that, in any linear, bilateral network consisting of many sources and impedances, current in any branch AB, is equal to current due to a single current source connected in parallel with a resistance impedance where, the single current source is the short circuit current flowing in the branch AB, and the parallel resistance is the total resistance measured by looking back into the network from the terminals AB. While measuring all the sources are to be replaced by their internal resistances.

Formula :

$$I_L = \frac{I_{sc} \cdot R_N}{(R_N + R_L)}, \text{ where } I_{sc} \rightarrow \text{short circuit current}$$

$$R_N \rightarrow \text{Norton Resistance}$$

$$R_L \rightarrow \text{Load Resistance}$$

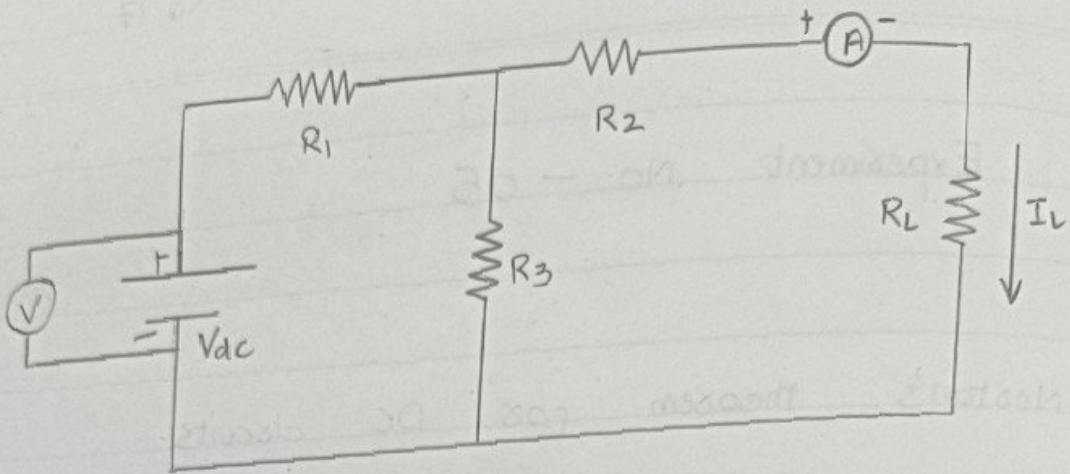


Fig. 5.1 → connection Diagram of Norton Theorem

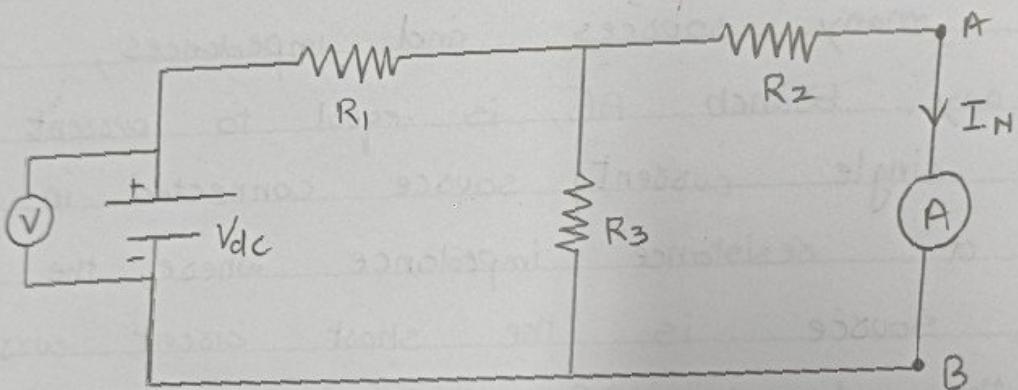


Fig. 5.2 → Calculation of  $I_{SC}$

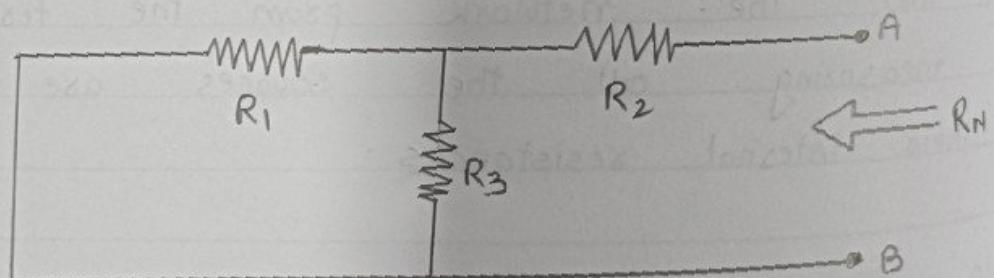


Fig. 5.3 → Measurement of  $R_N$

$$R_1 \rightarrow (100 \pm 1\%) \Omega$$

$$R_2 \rightarrow (517 \pm 1\%) \Omega$$

$$R_3 \rightarrow (100 \pm 1\%) \Omega$$

$$R_4 \rightarrow (330 \pm 1\%) \Omega$$

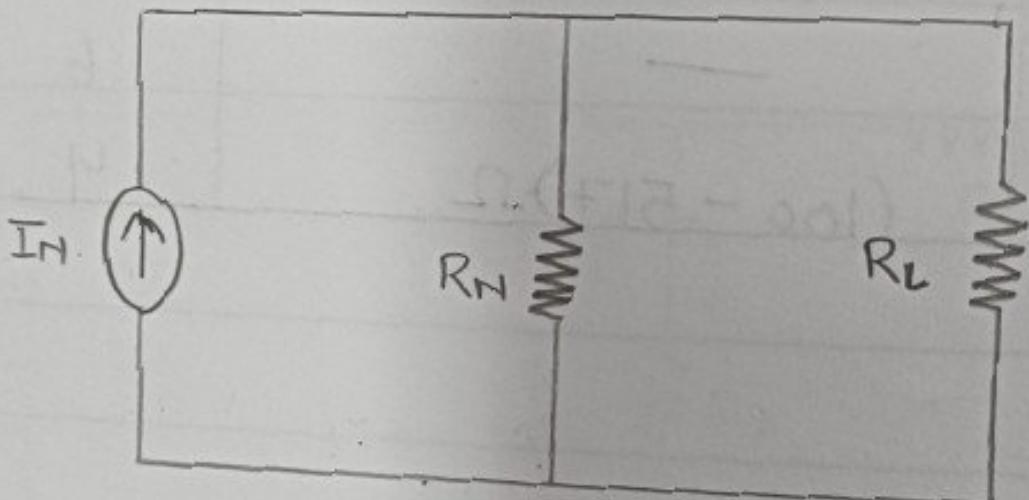
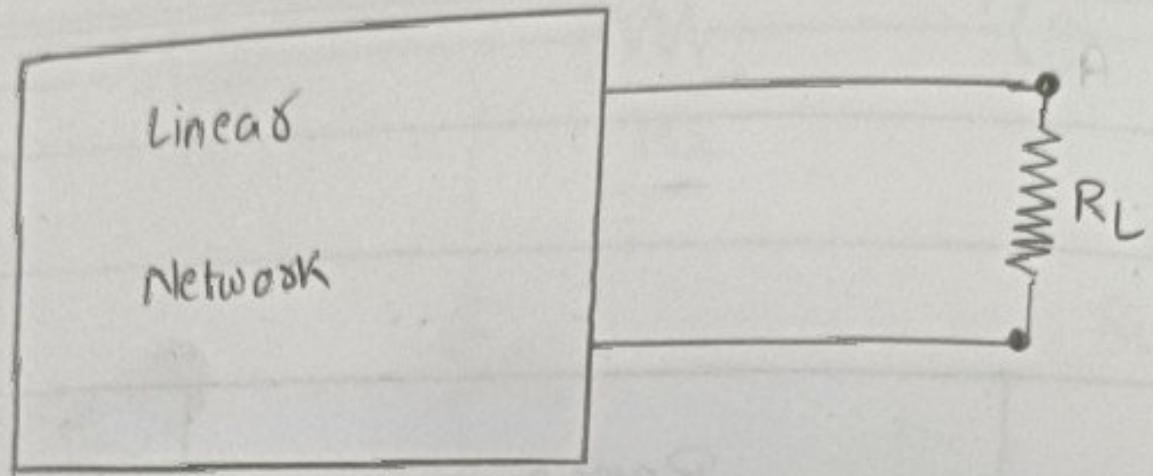


Fig. 5.4 → Norton's Equivalent Circuit

### Apparatus Required :

S. No.	Name	Range	Quantity
01>	DC Voltmeter	0 - 20V	1
02>	DC Ammeter	0 - 200 mA	1
03>	Breadboard	—	1
04>	connecting Wires	—	6
05>	carbon Resistors	(100 - 517) $\Omega$	4

### Procedure :

- 1> The circuit is connected as shown in Fig. 5.1.
- 2> Note the reading of ammeter which is load current in the circuit.
- 3> Find the short circuit current through the terminal AB when Load Resistance is short circuited (Fig. 5.2)
- 4> Measure the Norton's Resistance by using (Fig. 5.3)
- 5> Compute the current flowing through  $R_L$  (Fig. 5.4) using the equation

$$I_L = \frac{I_N R_N}{(R_N + R_L)}$$

And compare with First Reading.

## Observation Table :

S. No.	$V_{dc}$ (V)	$I_L$ (mA)	$I_N$ (mA)	$R_N$ ( $\Omega$ )	$R_L$ ( $\Omega$ )	$I_L = \frac{I_N \times R_N}{(R_N + R_L)}$ (mA)
01.	2	2.1	3.3	610	330	2.14
02.	4	4.2	6.6	610	330	4.28
03.	7	7.5	11.5	610	330	7.46
04.	10	10.7	16.5	610	330	10.70

## Conclusion :

Hence, Newton Theorem is verified for D.C. circuits.

## Precaution :

- 1> As the input is on DC supply, use only the DC meters.
- 2> Connect the DC meters with proper polarity.
- 3> Complete the circuit as per the diagram.
- 4> All connections must be tight and proper.

### Learning Outcomes :

- 1> We learnt to create circuit on breadboard.
- 2> We learnt colour coding of different resistors.
- 3> We learnt about Norton's Theorem and verified it practically.

### Applications :

It is widely used for circuit analysis simplification and to study circuit's initial - condition and steady-state response.

# EXPERIMENT NO: 06

**OBJECTIVE:** - To verify maximum power transfer theorem in DC circuits.

**THEORY:** Maximum power transfer theorem states that the load draws maximum power from the source, when the load resistance is equal to the internal resistance of the source.

At  $R_L = R_{th}$ , the power consumed by the load is maximum.

The power in the load is given by

$$\begin{aligned} P &= I_L^2 R_L = V_L^2 / R_L \\ &= V_L I_L \end{aligned}$$

## APPARATUS REQUIRED:

S. No.	Name	Range/Value	Quantity
1	DC Voltmeter		1
2	DC Ammeter		1
3	Breadboard		1
4	Connecting wires		6
5	Carbon resistors		2

**FORMULA:** Power  $P = I_L^2 R_L = V_L^2 / R_L$  watt

Where,  $I_L$  = Load current.

$R_L$  = Load resistance

$V_L$  = Voltage across the load

## CIRCUIT DIAGRAM:

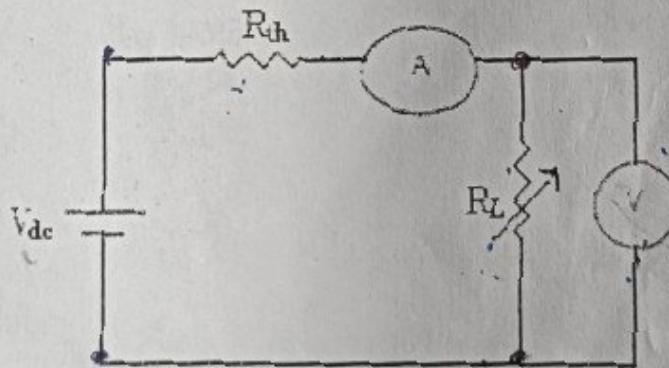


Fig. 6.1 Connection Diagram of Maximum Power Theorem

# Experiment No. 6

\* Aim: Verify Maximum Power Theorem

\* Theory: Load draws max power from the source, when the load resistance is equal to the internal resistance of the source.  
At  $R_L = R_{th}$ , power consumed is max

$$P = I_L^2 R_L = V_i I_L - V_L I_L$$

\* Apparatus Required:-

S.N.	Name	Range	Quantity
1.	DC Voltmeter	(0-20) V	1
2.	DC Ammeter	(0-200) mA	1
3.	Breadboard	-	1
4.	Connecting wires	-	6
5.	Carbon Resistors	(100-1500) Ω	5

\* Formula:  $P = V_i^2 / R_L = V_L I_L$  watt

**PROCEDURE:**

- The circuit is connected as shown in the Fig. 6.1.
- $R_{th}$  is fixed at some suitable value, for a particular value of  $R_L$  the ammeter (A) and voltmeter (V) reading are noted.
- By varying the value of  $R_L$  from  $R_L < R_{th}$  to  $R_L > R_{th}$ , the voltage across the load and current through the load are noted.
- Now the power is calculated by using the formula

$$P = I_L^2 R_L = V_L^2 / R_L = V_L I_L$$

- For each value of current  $I_L$  or  $V_L$ , take the value of  $R_L$  at the maximum power. If  $R_L$  value is equal to the internal resistance of source  $R_{th}$ , then the theorem is proved.

**OBSERVATION TABLE:**

S.No	Load Resistance ( $R_L$ ) ( $\Omega$ )	Voltage across load ( $V_L$ ) (Volts)	Current through load ( $I_L$ ) (mA)	$P_L = V_L I_L$ (W)	$R_{th}$ ( $\Omega$ )

**RESULTS:** It is found that power consumed is maximum when  $R_L$  becomes equal to  $R_{th}$ . This verifies the maximum power transfer theorem.

**LEARNING OUTCOMES:** (to be filled by student)

**APPLICATIONS:** (to be filled by student)

**PRECAUTION:**

- The load resistance  $R_L$  is varied from  $< R_{th}$  to  $> R_{th}$ .
- Internal resistance of the source should be measured before going to the experiment.
- All connections should be tight.

**VIVA QUESTION:**


- What is max power transfer formula?
- What is the field of application of this theorem?
- What is electric network?
- What is necessary to know the polarity of voltage drop across a resistance?
- What is the reason that terminal voltage is less than emf?
- What is the resistance of ideal voltage source?
- When will the power extracted from a ckt is maximum

10/04/23



Ni  
Title

## Electrical - 06

Graph

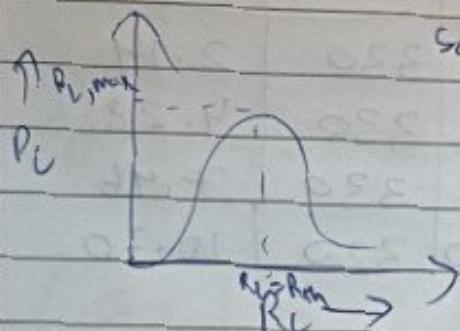

Scalby

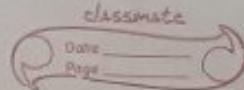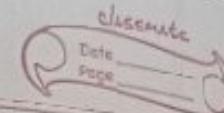

S.No	Load Resistance $R_L$	Voltage across load $V_L(V)$	Current $I_L(MA)$	$P_L = V_L \cdot I_L$	$R_{th}$
1	100	0.73	8.2	5.986	330
2	330	1.71	5.4	9.234	330
3	750	2.42	3.3	7.986	330
4	1500	2.88	1.9	5.472	330

$$R_1 \rightarrow (100 \pm 1\%) \Omega$$

$$R_2 \rightarrow (330 \pm 1\%) \Omega$$

$$R_3 \rightarrow (750 \pm 1\%) \Omega$$

$$R_4 \rightarrow (1500 \pm 1\%) \Omega$$

$$R_S \rightarrow (330 \pm 1\%) \Omega$$